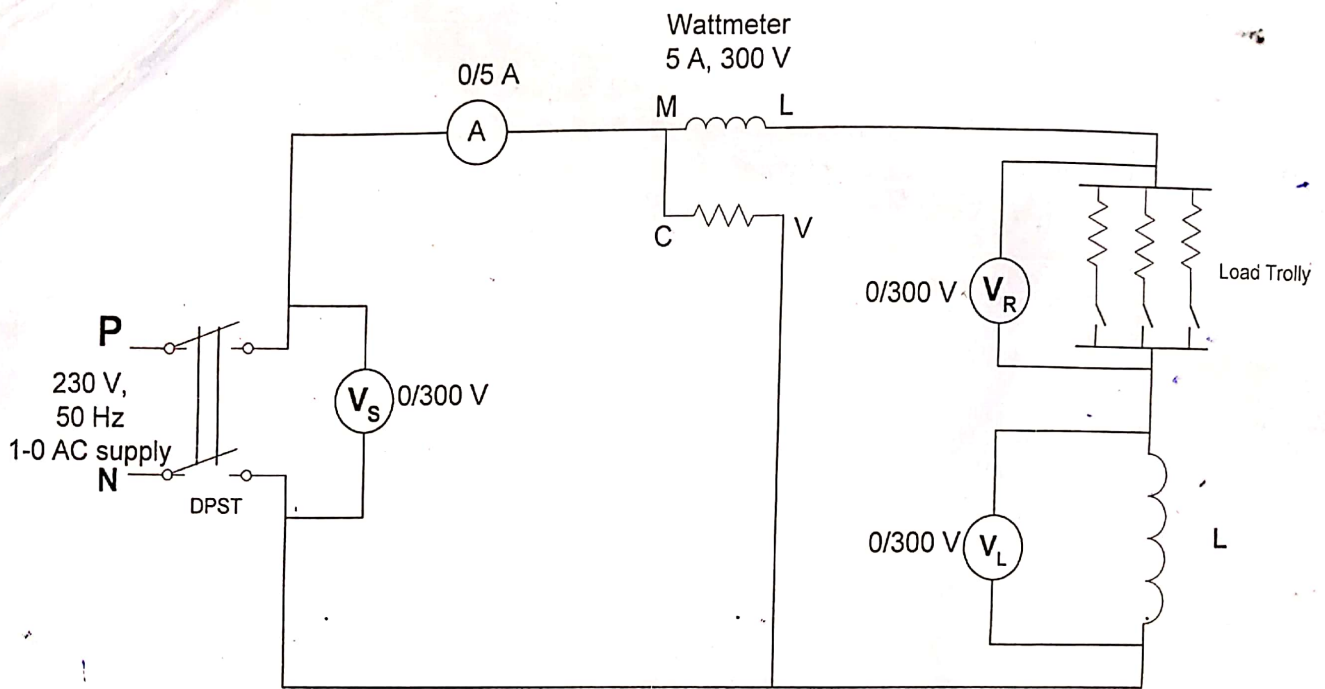


MEASUREMENT OF POWER IN R-L SERIES CIRCUIT

CIRCUIT DIAGRAM



OBSERVATION TABLE

I (AMP)	V_R (VOLT)	V_L (VOLT)	V_s (VOLT)	W (WATT)

Measurement of Power in 3-Phase Circuit

