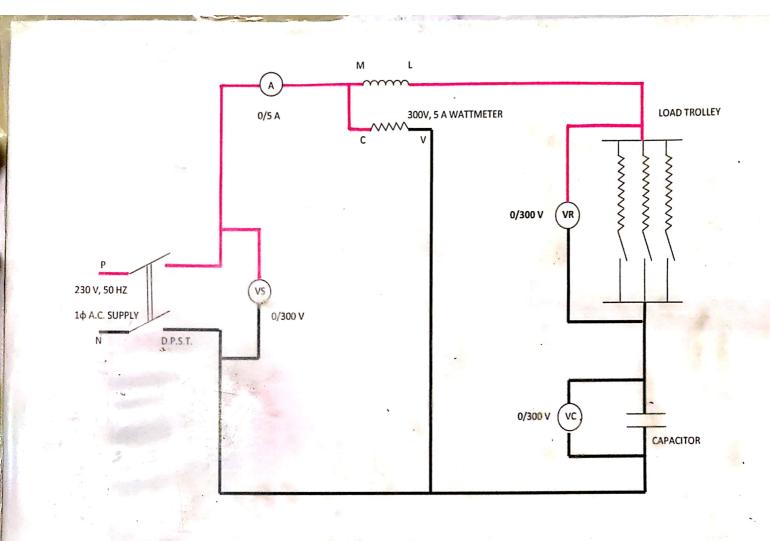


Scanned by CamScanner



POWER IN R-C SERIES CIRCUIT

OBSERVATION TABLE

5.	4.	.ω,	2.	1.	No.	Sr.
	•	7 .		,	In Amps	Circuit Current
	×.				Reading in Watts	Wattmeter
					Supply V	Vo
			,		Resistance V _R	Voltage in Volts Across
					Capacitance V _c	S